

1. Consider a 4-bit carry lookahead adder which has two levels with two 2-bit groups on first level.
 - (a) Please find out the formula of G_0 , G_1 , P_0 , P_1 , C_1 , and C_2 when adding two unsigned 4-bit numbers and a carry-in, say c_0 . (Please describe your answer in terms of $p_0 \sim p_3$, $g_0 \sim g_3$ and c_0).
 - (b) Compare the number of gate delays for the above carry lookahead adder with a 4-bit ripple carry adder.

2. Calculate the time necessary to perform a multiply of two 32-bit integers. Please
 - (a) Use the optimized multiplication block diagram.
 Assume the operations of multiplier-bit0 checking and step 1a are merged as: add the multiplicand ANDed with bit0 of multiplier. So this step is always performed.
 Assume each step of operation takes 7 time units.
 - (b) Use the fast multiplication hardware with 31 adders. Assume an adder takes 7 time units.

3. Please make a comparison and list the difference between the two versions of the multiplication block diagrams.

4. (a) Complete the table below using 1-bit Booth's algorithm to compute 3×-4 (i.e., $0011_2 \times 1100_2$)
 (b) Some particular bit patterns may make Booth's algorithm slow. Give an example and explain.

Iteration	Multiplicand	Product
0 (Initial)	0011	
1		
2		
3		
4		

1 (a)

$$\mathbf{P0 = p1 \ p0}$$

$$\mathbf{P1 = p3 \ p2}$$

$$\mathbf{G0 = g1 + p1 \ g0}$$

$$\mathbf{G1 = g3 + p3 \ g2}$$

$$\mathbf{C1 = G0 + P0 \ c0}$$

$$\mathbf{C2 = G1 + P1C1 = G1 + P1 \ G0 + P1 \ P0c0}$$

(b) 4-bit ripple carry: 8 gate delay

4-bit carry lookahead: 2+2+1=5 gate delay

2. (a) add: 7tu shift: 7tu check for end: 7u
 $3 \times 7(\text{tu}) \times 32(\text{loops}) = 672 \text{ tu}$
 (b) 5 level \times 7 tu = 35 tu

3	Multiplicand is 64 bits	Multiplicand is 32 bits
	Multiplicand don't shift	Multiplicand don't shift
	ALU is 64-bit	ALU is 32-bit
	Product don't shift	Product must shift right
	Multiplier is independent 32-bits	Multiplier is in low 32-bit of product

4.

Iteration	Multiplicand	Product
0 (initial)	0011	0000 1100 0
1	0011	0000 0110 0
2	0011	0000 0011 0
3	0011	1110 1001 1
4	0011	1111 0100 1

NOP/shift
 NOP/shift
 Sub/shift
 NOP/shift

- (b) With many short 1's in the sequence
 e.g., 10101010